# NATIONAL RADIO ASTRONOMY OBSERVATORY Green Bank, West Virginia

Electronics Division Internal Report No. 38

A FERRITE SWITCH DRIVER

James L. Dolan

OCTOBER 1964

NUMBER OF COPIES: 75

#### A FERRITE SWITCH DRIVER

#### James L. Dolan

### Objective

To design and build a 400 cycle per second reference and power driver for the ferrite switch in the 3.2 mm receiver (project 217).

## Specifications

Drive current ----- 75-100 mA to an inductive level

Frequency ----- 400 Hz square wave

Temperature range-- 0-50 °C

Frequency range --- ± 10 Hz

Rise time ----- Better than 100  $\mu$ s

### Discussion

The above specifications can be met by conventional means with one exception. This is the rather difficult requirement for a square current waveform to an inductive load. This requirement was met by adapting a circuit originally designed by MIT, Lincoln Lab.

This concept utilizes the transient voltage from one inductor to start current flow in another. The equivalent circuit for the drive current is shown in Figure 1.


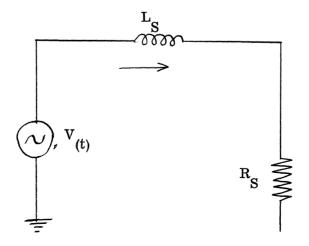


Figure 1

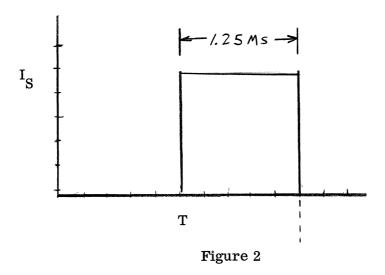 $L_S^{}$  is the switch industances, and  $R_S^{}$  is the DC resistance of the switch. It was desired that the current  $(I_S^{})$  be a step function as shown in Figure 2.



It can be shown that if  $V_{(t)}$  (applied voltage) is a step function  $U_{(t)} = E$ , then  $i_{(t)}$  is an exponential function of the circuit time constant  $\frac{L}{R}$ .

$$i_{(t)} = \frac{E}{R} \begin{pmatrix} -\frac{R}{L} t \\ 1 - e \end{pmatrix}$$
 (1)

This is the familiar equation for current flow at any time (t) in an R-L circuit. If the current i(t) is to approach the steady state value of  $\frac{E}{R}$ , then the applied electromotive force (EMF) cannot be a step function but must vary in some prescribed manner with time. From equation (1), with  $i_{(t)} = I$ ,  $V_{(t)} = \frac{E}{-\frac{R}{L}t}$ .  $V_{(t)}$  will then have the form shown in figure 3.

$$V_{(t)}$$

Locus of  $\frac{E}{-\frac{R}{L}t}$ 

Figure 3

If  $i_{(t)}$  is to rise instantaneously to I (steady state), then  $V_{(t)}$  must rise to infinite at t=0. Practically, this is not possible since the switching time is not zero. The finite switching time limits  $V_{(t)}$  to a finite value.

The equivalent circuit utilizing the concept of opposing inductors is shown in figure 4.

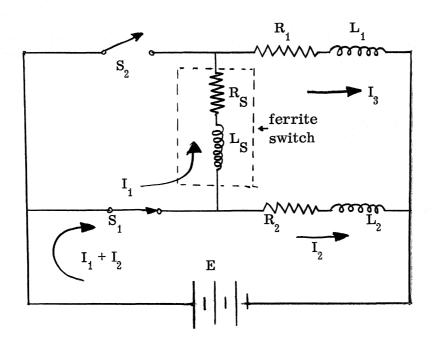


Figure 4

In the circuit,  $S_1$  and  $S_2$  are transistor switches. When  $S_1$  is opened and  $S_2$  is closed, the transient voltage around the closed loop is of opposite polarity. If the auxiliary inductors ( $L_2$  and  $L_3$ ) have the correct inductance, the transient voltages will cancel and the current  $i_{(t)}$  will rise to its steady state value instantaneously. The equation for  $L_2$  and  $L_3$  is

$$L_2 = L_3 = L_S \left( \frac{2I_S}{I_{max} - I_S} \right)$$
 (2)

The known parameters in the circuit are  $L_S$  and  $R_S$  and the current,  $I_{S^*}$ . From these parameters and the value of applied voltage E,  $L_2$  and  $L_3$  can be calculated.

The schematic for the completed circuit is shown in figure 5 (appendix). Circuit operation is as follows:

Transistors  $Q_1$ ,  $Q_2$  and  $Q_3$  are used in a conventional R-C phase shift oscillator designed to run at 400 Hz. In order to eliminate any quadrature component in the phase detector output, the oscillator frequency is adjustable  $\pm$  10 Hz around 400 Hz. This enables the operator to center the reference signal in the pass band of the narrow filter preceding the phase detector. Transistor  $Q_4$  is used as a high input impedance emitter-follower to prevent oscillator loading. Diodes  $D_1$  and  $D_2$  are zener clippers that change the oscillator sine wave output to a near square wave.  $Q_5$  and  $Q_6$  comprise an overdriven squaring circuit. The output from  $Q_6$  is a square wave with an amplitude of 20 volts peak-to-peak and a rise time of approximately 10-15 microseconds.  $Q_7$  and  $Q_8$  are compound connected transistors used as a power driver for one of the high voltage output transistors.  $Q_9$  and  $Q_{10}$  are also compound connected and act as an inverter and power driver for the other output transistor.

#### Measured Circuit Characteristics

Frequency----- 400 Hz adjustable  $\pm$  10 Hz

Stability -----  $\pm 3$  Hz for 24 hours

Operating temperature range - 0-50 °C

Rise time ----- Less than 100  $\mu s$ 

Power output ----- 1.5 watts (100 mA - 150  $\Omega$  load).

